

## 5.2 Circuit diagrams

Describe the components of the circuits, and whether the bulb will light and why.

	
	
	
	
	